

# Hardware Assignment 1

Jaskaran Singh Bhalla (2021TT11139)

Saurabh Arge (2022CS11610)

## Problem

- Design a combinational circuit and implement.
- Take a 4-digit decimal/hexadecimal number ( 4-bit number) from switches in the Basys3 board.
- Display output on the 4-seven segment displays on the board.
- Display the output on a single board.

## Approach

- **Assumption**
  - We have represented 4-bits using the hexadecimal system.
- **Analysis**
  - We understood the functioning of a single digit on one of the four seven segment displays including the connections between 7 cathodes and 1 anode.
  - We figured out how input is taken using the switch from the Basys3 board.
- **Calculations**
  - We created the k-maps for each of the 7 leds (cathodes) and derived the combinational logic to display 16 different outputs on the display using 4-bit input given through switches.
  - The **Seven K-maps** with their derived combination logic are given below.
  - We have derived the combination logics for each led and then taken negation of each logic in implementation through code because in the problem statement Active mode is taken to be 0 and inactive state is taken as 1.
  - **ACTIVE = 0, INACTIVE = 1**

## Implementation

- We wrote the code using combinational logic in VHDL and generated the bitstream and ran the code on the Basys3 board.
- For a single display we created 4 variables and with 3 of the variables set to inactive (1) state indicating that the display is off and 1 variable is marked in active state (0) indicating that 1 display is on.

## Results

- We manually confirmed all the outputs on the Basys3 board.
- With no flickering all the displays , correctly displayed the output
- Later using the 4 variable logic we were able to display the 4-bit digit on a single display only.
- Images of the output have been attached below.

## Concluding Remarks

It was a great experience learning VHDL and implementing the design for the 7-segment decoder on our own. Understanding the display LED logic using k-maps and implementing it practically was a really nice experience.

## K-Maps

**Output LED a**

		Output LED a				
		00	01	11	10	
		00	1	0	1	1
		01	0	1	1	1
		11	1	0	1	1
		10	1	1	0	1

**Combinational Logic :**

$$a \Rightarrow A'B'C'D' + A'BC'D + AB'C'D + AB'CD' + AC'D' + A'B'C + BC$$

**Output LED b**

		Output LED b				
		00	01	11	10	
		00	1	1	1	1
		01	1	0	1	0
		11	0	1	0	0
		10	1	1	0	1

**Combinational Logic :**

$$b \Rightarrow A'BC'D' + A'BCD + AB'CD' + AB'C'D' + AC'D + A'B'$$

### Output LED c

		Output LED c				
		00	01	11	10	
CD	AB	00	1	1	1	0
		01	1	1	1	1
CD	AB	11	0	1	0	0
		10	1	1	1	1

### Combinational Logic :

$$c \Rightarrow ABC'D + A'B'CD + A'B'C' + AB' + A'B$$

### Output LED d

		Output LED d				
		00	01	11	10	
CD	AB	00	1	0	1	0
		01	0	1	0	1
CD	AB	11	1	1	0	1
		10	1	1	1	0

### Combinational Logic :

$$d \Rightarrow A'B'C'D' + A'BC'D + AB'CD + A'B'C + BCD' + AC'$$

### Output LED e

		Output LED e				
		00	01	11	10	
CD	AB	00	1	0	0	1
		01	0	0	0	1
11	11	1	1	1	1	1
10	10	1	0	1	1	1

### Combinational Logic :

$$e \Rightarrow A'B'C'D' + AB'C'D' + A'CD' + AB'C + AB$$

### Output LED f

		Output LED f				
		00	01	11	10	
CD	AB	00	1	0	0	0
		01	1	1	0	1
11	11	1	0	1	1	1
10	10	1	1	1	1	1

### Combinational Logic :

$$f \Rightarrow A'B'C'D' + A'BCD' + ABC'D' + A'BC' + ABC + AB'$$


### Output LED g

		Output LED g			
		00	01	11	10
AB	CD	00	0	1	1
		01	1	1	1
AB	CD	11	0	1	1
		10	1	1	1

### Combinational Logic :

$$g \Rightarrow A'BCD' + AB'C'D' + A'B'C + A'BC' + AC'D + AC$$
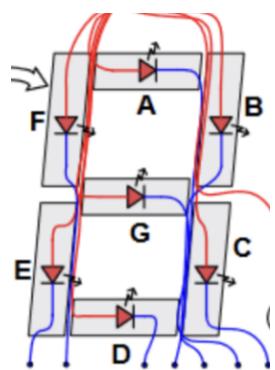
### Mapping of LEDs to VHDL code variables



- a = Combination Logic for LED A
- b = Combination Logic for LED B
- c = Combination Logic for LED C
- d = Combination Logic for LED D
- e = Combination Logic for LED E
- f = Combination Logic for LED F
- g = Combination Logic for LED G

## Visual Outputs

Input format : ABCD

For Example , Take a 4-bit digit with numeric value = 5

A = 0, B = 1, C = 0, D = 1

It will display 5.

<b><i>Input</i></b>	<b>Visual</b>
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	B
1100	C
1101	D
1110	E
1111	F

## Basys3 Board Output

